

## DIGITAL ELECTRONICS EXPERIMENT - 2

JUNAID • GIRKAR  
60004190057

\* **AIM:** To implement the logic functions i.e. AND, OR, NOT, EX-OR, EX-NOR and a logical expression with the help of NAND and NOR universal gates respectively.

\* **THEORY:** Logic gates are electronic circuits which perform logical functions on one or more inputs to produce one output. There are seven logic gates. When all the input combinations of a logic gate are written in a series and their corresponding outputs written along them, the input combination is called Truth Table.

### 1. NAND GATE AS UNIVERSAL GATE :

- NAND gate is actually a combination of two logic gates (AND followed by NOT). So, the output is the complement of the AND gate. This gate can have minimum 2 inputs; output is always one.
- By using only NAND gates, we can realize all logic functions: AND, OR, NOT, X-OR, X-NOR, NOR. So this gate is also called a universal gate.

### → NAND gates as NOT gate


- A NOT produces the complement of the input. It can have only one input, tie the inputs of a NAND gate together. It will work as a NOT gate with the output.

• **EXPRESSION :**

$$Y = (A \cdot A)'$$

$$= A'$$

• DIAGRAM :

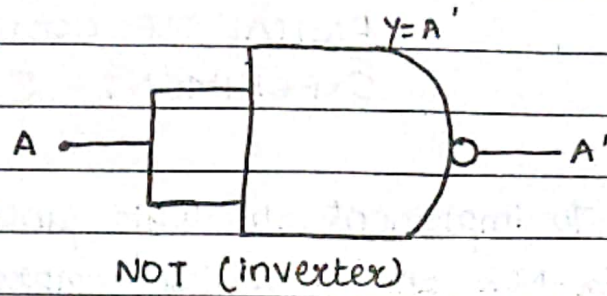

TRUTH TABLE:


Input	output
A	A'
0	1
1	0

→ NAND gates as AND gate.

• A NAND produces complement of the AND gate. So, if the output of a NAND gate is inverted, overall output will be that of AND gate.

• EXPRESSION :  $Y = ((A \cdot B)')' = A \cdot B$   
 $Y = A \cdot B$

• DIAGRAM :

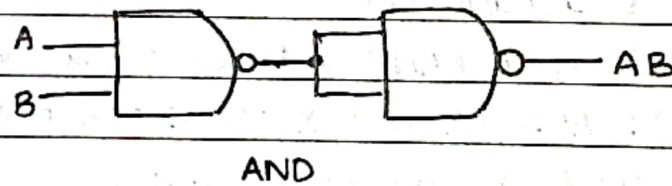


TRUTH TABLE:

Input		Output
A	B	$F = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1



→ NAND gates as OR gate

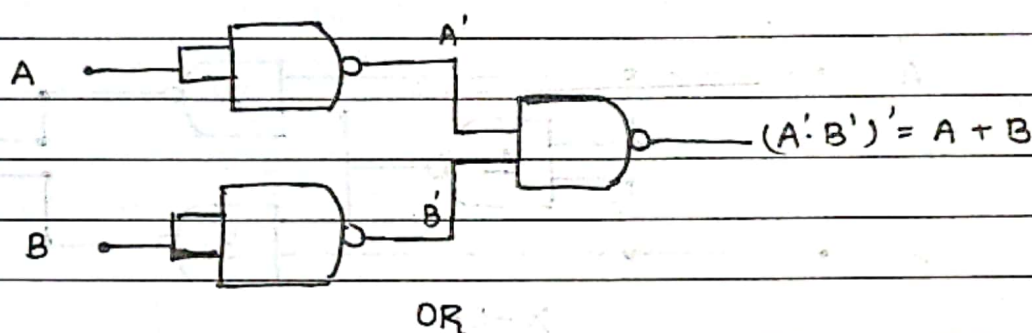- From De Morgan's theorem:  $(A \cdot B)' = A' + B'$   
 $(A'B')' = A'' + B'' = A + B$
- So give the inverted outputs to the NAND gate, obtain OR operation at output.
- EXPRESSION:  $Y = A + B$
- DIAGRAM:



TRUTH TABLE:

A	B	$X = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

→ NAND gates as EX-OR gate

- The output of two input EX-OR gate is shown by  $Y = A'B + AB'$

Gate No	INPUT	OUTPUT
1	A, B	$(AB)'$
2	A, $(AB)'$	$(A(AB)')'$
3	$(AB)'$ , B	$(B(AB)')'$
4	$(A(AB)')'$ , $(B(AB)')'$	$A'B + AB'$

The output from gate 4 is the overall output of the configuration.

$$Y = ((A(AB)')') \cdot (B(AB)')') = (A(AB)')'' + (B(AB)')''$$


$$Y = A(AB)' + B(AB)' = (A(A'+B)') + (B(A'+B'))$$

$$Y = AA' + AB' + BA' + BB' = 0 + AB' + BA' + 0$$

$$Y = AB' + A'B$$

• EXPRESSION:  $Y = AB' + A'B$

• DIAGRAM

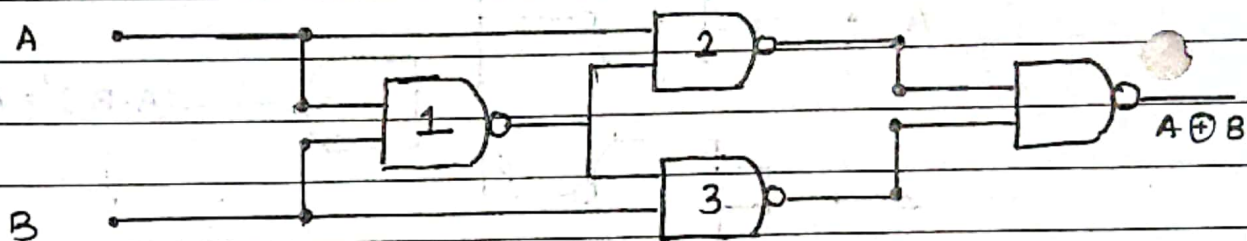

X-OR


TRUTH TABLE

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

→ NAND gates as Ex-NOR gate

• Ex-NOR gate is the Ex-OR gate followed by the NOT gate. so given the output of Ex-OR gate to a NOT gate, overall output is that of Ex-NOR gate.

• EXPRESSION:  $Y = AB + A'B'$

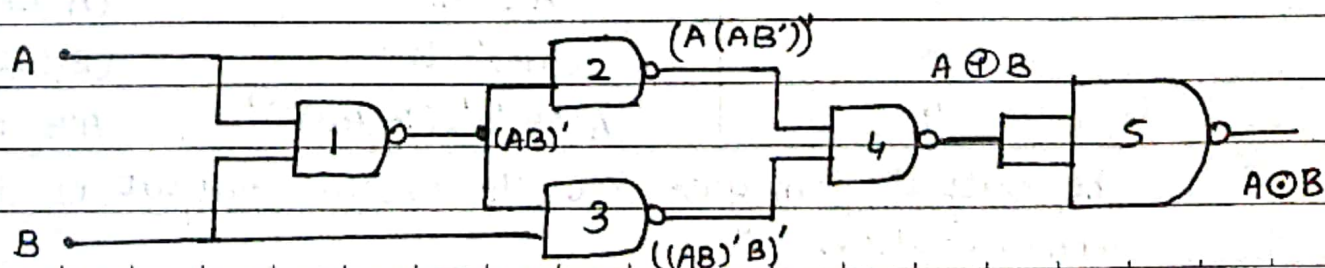

X-NOR



• TRUTH TABLE :


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

→ IMPLEMENTING THE SIMPLIFIED FUNCTIONS WITH NAND GATES ONLY

• EXPRESSION:  $F = ((C \cdot B \cdot A)'(D \cdot C \cdot A)'(C \cdot B \cdot A)')'$

- The entire expression is inverted and we have three terms ANDed. This means that we must use a 3-input NAND gate. Each of the three terms is itself a NAND expression. Finally, negated single terms can be generated with a 2-input NAND gate acting inverted.
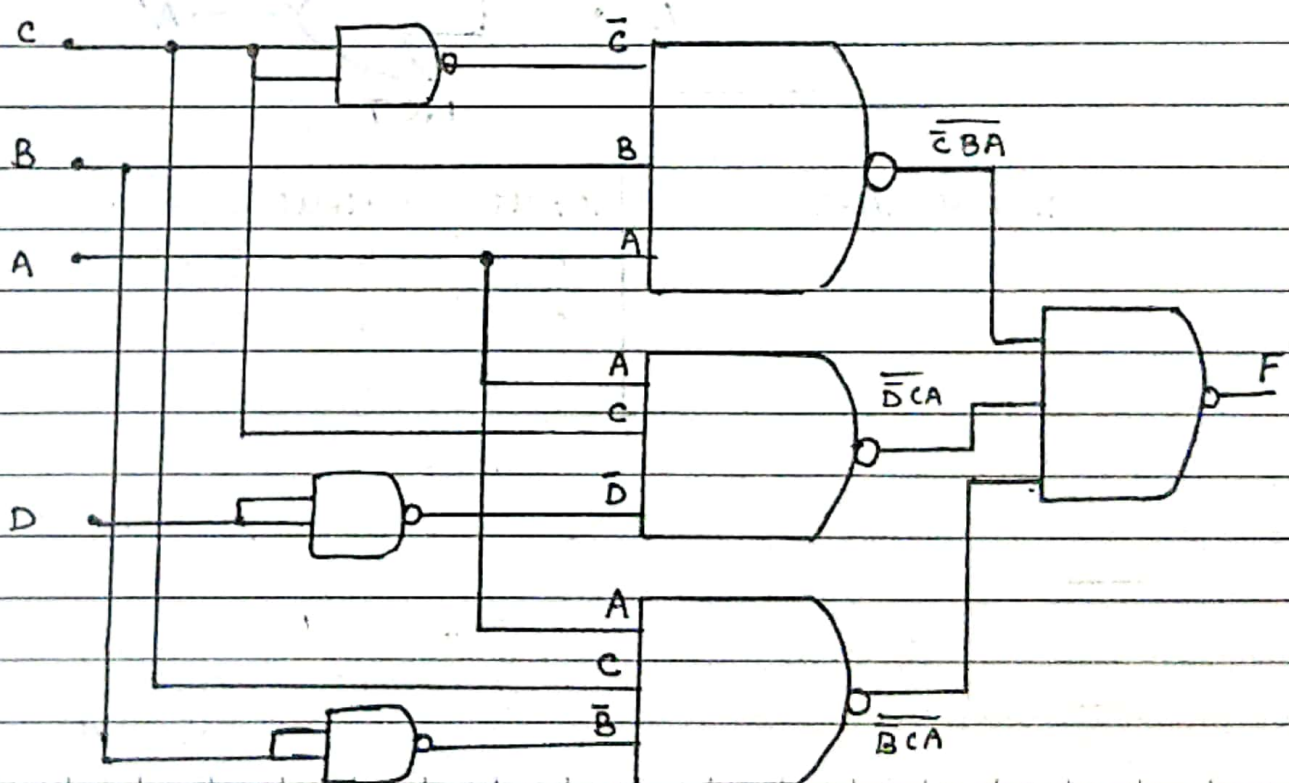
$$F = \overline{(\overline{C} \cdot B \cdot A)(\overline{D} \cdot C \cdot A)(C \cdot \overline{B} \cdot A)}$$




## 2. NOR GATE AS UNIVERSAL GATE

- NOR gate is actually a combination of two logic gates: OR gate followed by NOT gate. So its output is complement of the output of an OR gate. This gate can have minimum two inputs; output is always one. By using NOR gates, we can realize all logic functions: AND, OR, NOT, EX-OR, EX-NOR, NAND. So, this gate is also called a universal gate.

→ NOR gates as NOT gate :

- A NOT produces complement of the input. It can have only one input, and after trying the inputs of a NOR gate together, it will work as a NOT gate.
- EXPRESSION :  $Y = (A + A)' = A'$

• DIAGRAM :

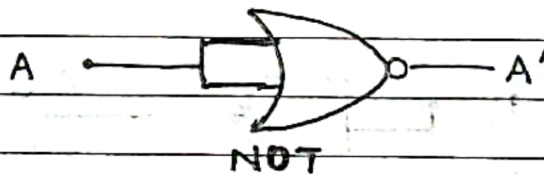

TRUTH TABLE :


INPUT	OUTPUT
A	A'
0	1
1	0



→ NOR GATES AS OR GATE :

- A NOR produces complement of OR gate. So, if the output of a NOR gate is inverted, overall output will be that of an OR gate.
- EXPRESSION :  $Y = ((A+B)')' = A+B$

• DIAGRAM :

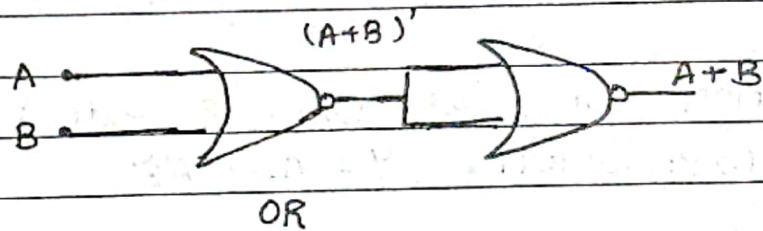

• TRUTH TABLE

A	B	$X = A+B$
0	0	0
0	1	1
1	0	1
1	1	1


→ NOR GATES AS AND GATE :

- By De Morgan's Law :  $(A+B)' = A'B'$   
 $(A'+B')' = A \cdot B$

so give the inverted inputs to a NOR gate, obtain AND operation at output

- EXPRESSION :  $Y = A \cdot B$

• DIAGRAM :

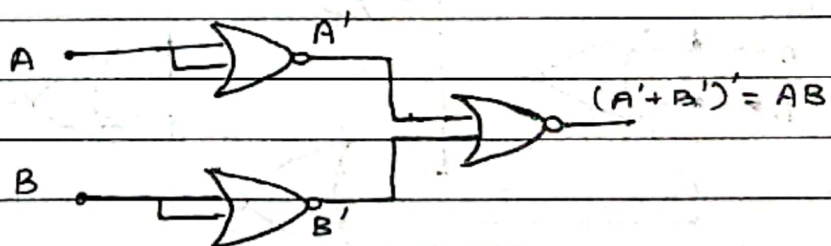

AND

TRUTH TABLE:

INPUT		OUTPUT
A	B	$F = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

→ NOR gates as Ex-NOR gate:

• EXPRESSION:  $Y = AB + A'B'$

Gate No	Inputs	output
1	$A \cdot B$	$(A+B)'$
2	$A \cdot (A+B)'$	$(A + (A+B)')'$
3	$(A+B)'.B$	$(B + (A+B)')'$
4	$(A + (A+B)')' \cdot (B + (A+B)')'$	$AB + A'B'$


$$Y = ((A + (A+B)')')' \cdot (B + (A+B)')')' = (A + (A+B)')(B + (A+B)')$$

$$Y = (A + A')(A + B')(B + A')(B + B') = A(B + A') + B'(B + A')$$

$$Y = AB + AA' + B'B + B'A' = AB + B'A'$$

$$Y = AB + A'B'$$

DIAGRAM

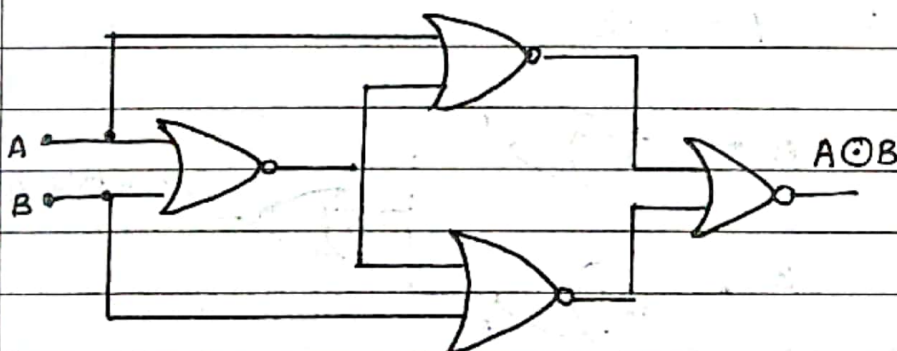

X-NOR


TRUTH TABLE

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1



→ NOR gates as Ex-OR gate :

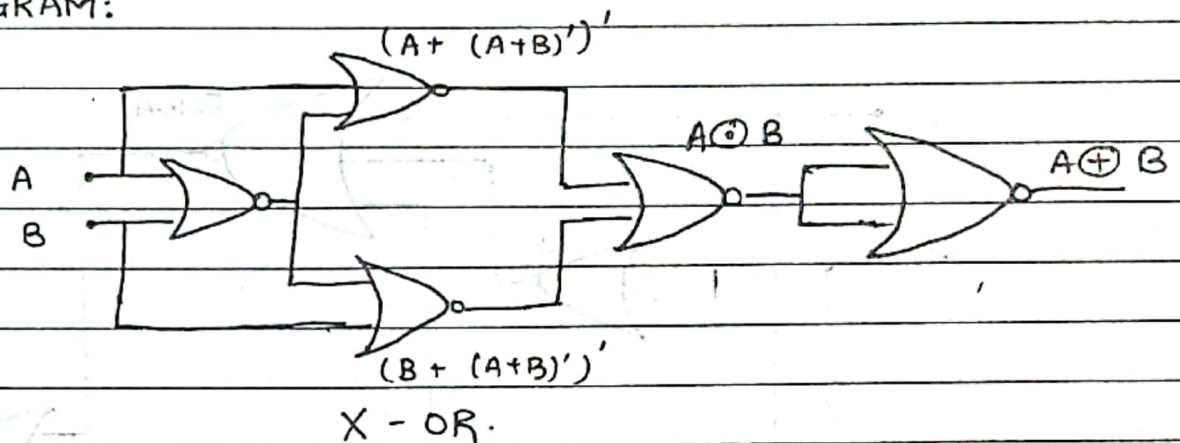- Ex-OR gate is actually Ex-NOR gate followed by NOT gate. So give the output of Ex-NOR gate to a NOT gate, overall output is that of an Ex-OR gate.
- EXPRESSION :  $Y = A'B + AB'$
- DIAGRAM:



• TRUTH TABLE

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

→ CONSTRUCTING A CIRCUIT WITH NOR GATES ONLY

•  $F = ((C \cdot \bar{B} \cdot A) + (D \cdot \bar{C} \cdot A) + (C \cdot \bar{B} \cdot A))' )'$

• DIAGRAM :

