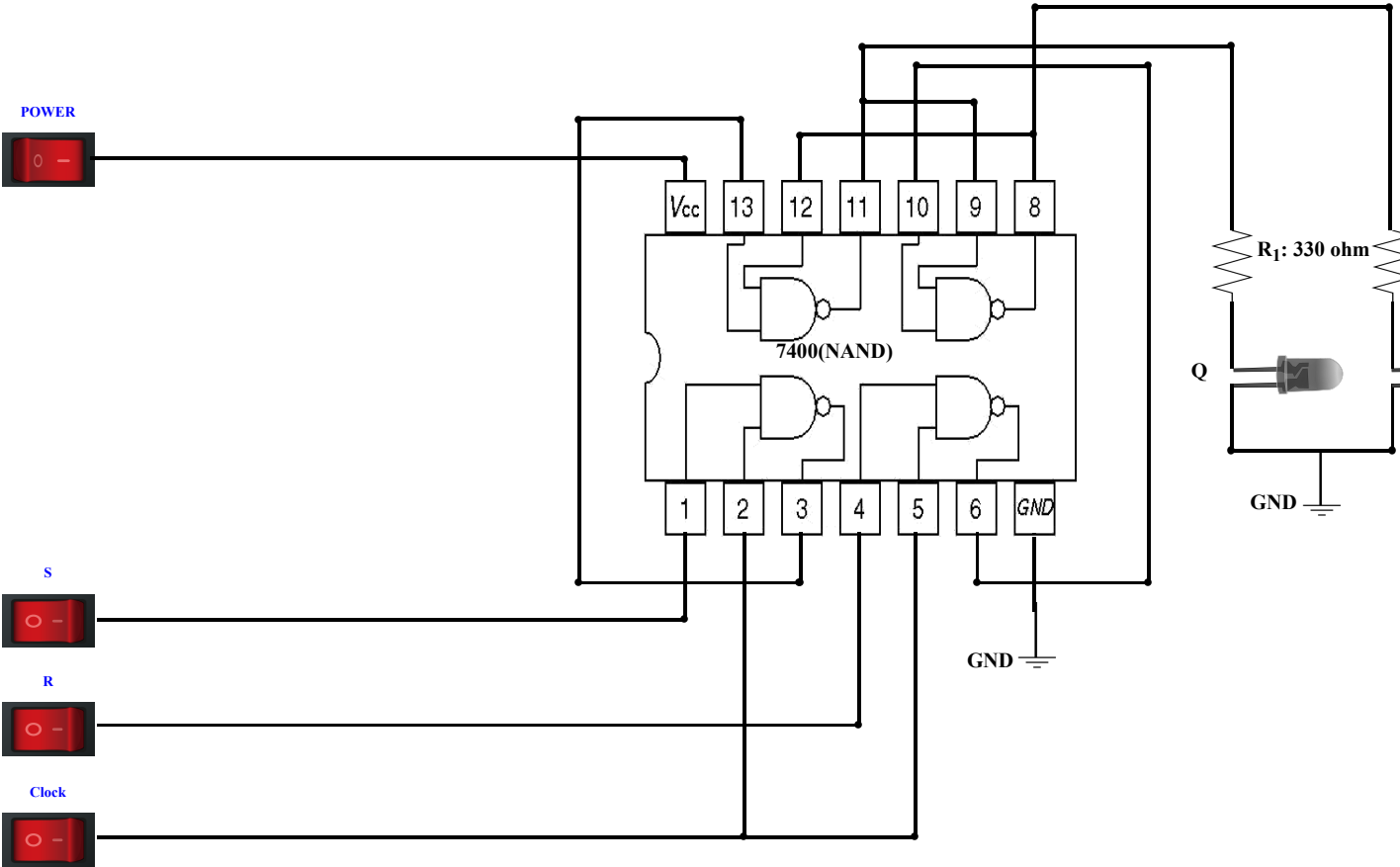


INSTRUCTIONS

Experiment to perform SR Flip Flop on kit



TRUTH TABLE				PRINT		Add		
Serial No.	clock	S	R	Q(n-1)	Q̄(n-1)	Q	Q̄	Remark
1	0	0	0	X	X	0	1	No Change
2	1	0	0	0	1	0	1	No change
3	1	0	1	0	1	0	1	Reset
4	1	1	0	0	1	1	0	set
5	1	1	1	1	0	0	0	INVALID

