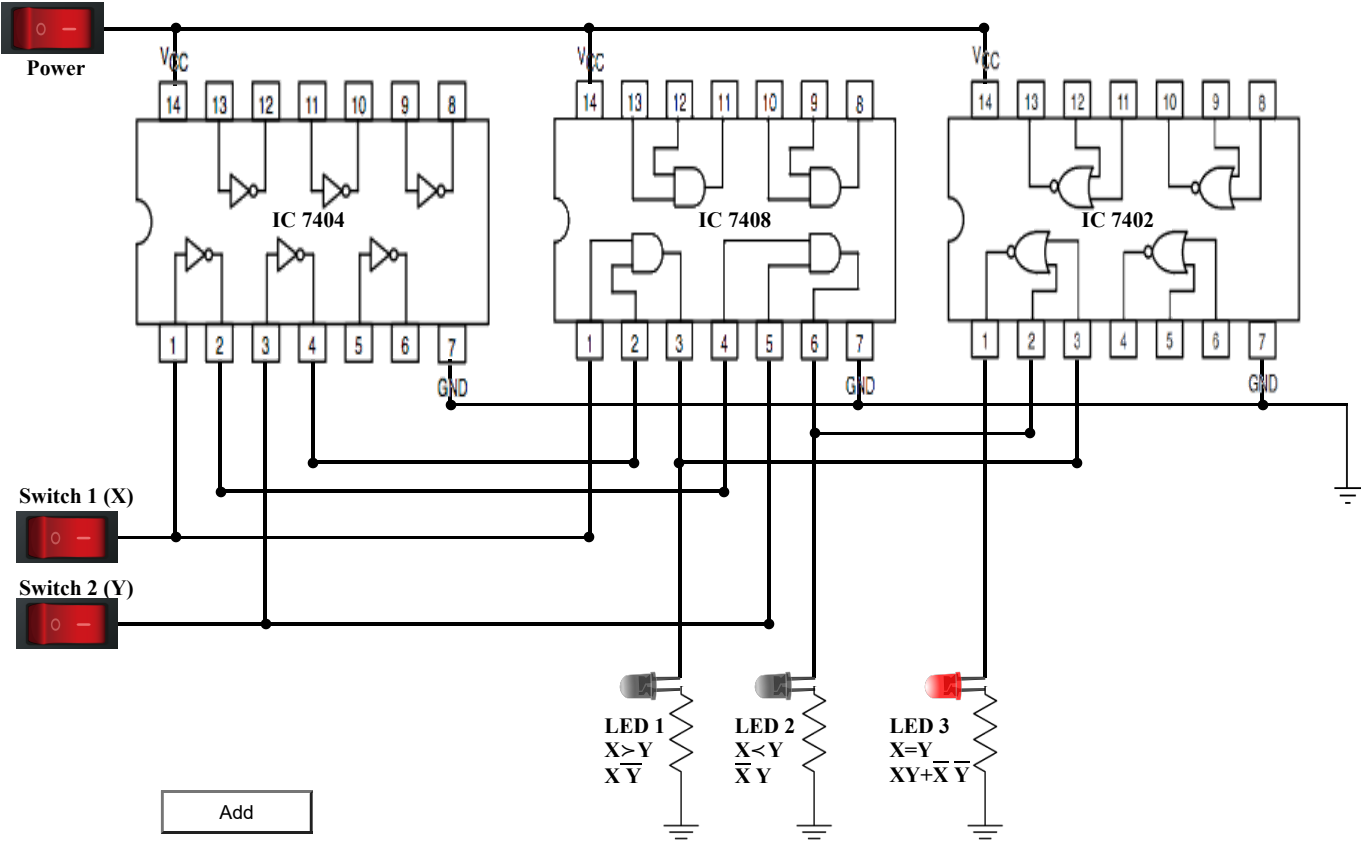


Instructions

Construction of 1-Bit Comparator and verification of its operation

Print



Add

TRUTH TABLE

Serial No.	X	Y	X > Y	X < Y	X = Y
1	0	0	0	0	1
2	0	1	0	1	0
3	1	0	1	0	0
4	1	1	0	0	1