

DE TT2

Q1

ANS



RACE AROUND CONDITION IN JK FLIP-FLOP

For JK flip-flop, if $J=K=1$, and if $clk=1$ for a long period of time, then the output will toggle as long as clk is high, which makes the output of the flip-flop unstable or uncertain. This problem is called race around condition in J-K flip-flop. The whole problem can be avoided by ensuring that the clock is at logic '1' only for a very short time. This introduced the concept of master slave JK flip-flop.

The master slave flip-flop is basically a combination of two JK flip-flops connected together in a series configuration. Out of these, one acts as the "MASTER" and the other as a "SLAVE". The output from the master flip-flop is connected to the two inputs of the slave flip-flop, whose output is fed back to inputs of the master flip-flop.

In addition to these flip-flops, the circuit also includes an inverter. The inverter is also connected to clock pulse in such a way that the inverted clock pulse is given to the slave flip-flop.

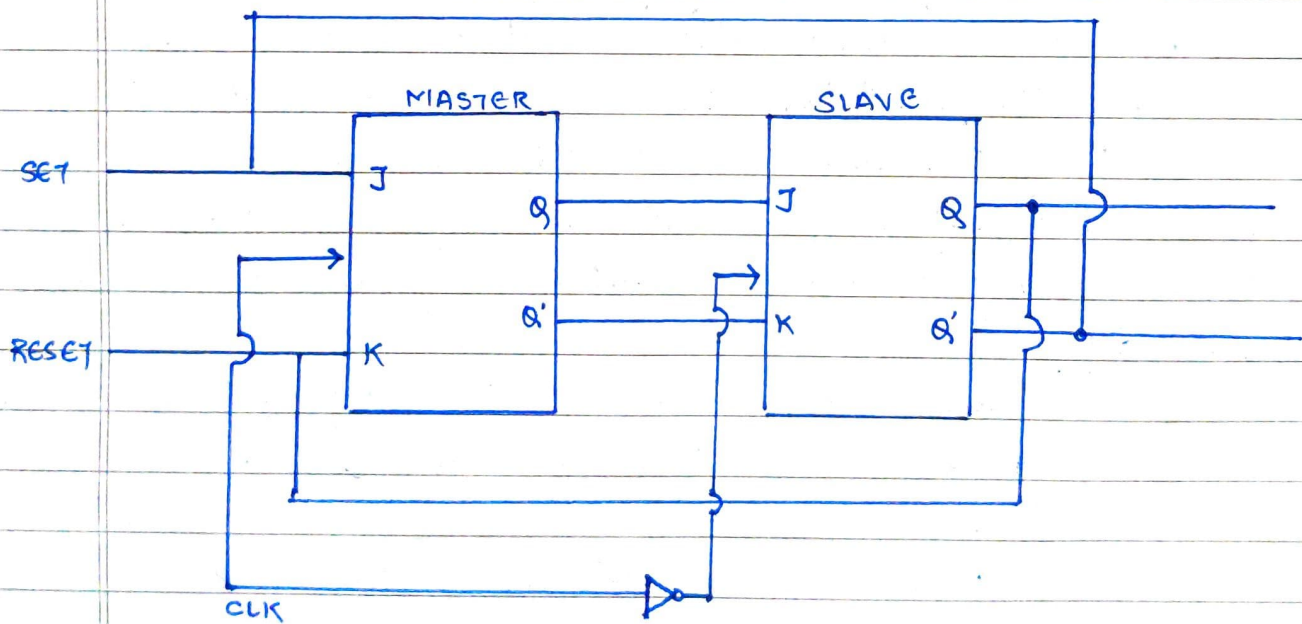 In other words if clock pulse = 0 for a master flip-flop, then clock pulse = 1 for a slave flip-flop and if clock pulse = 1 for master flip-flop then it becomes 0 for slave flip-flop.



Q2

ANS STEP 1: Since we have to design MOD-9 counter, 4 flip-flops are needed

STEP 2: TRUTH TABLE

State	Flip-flop output				output of Reset logic
	Q _D	Q _C	Q _B	Q _A	
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	0

States 0 to 8 are valid states and output of reset logic is inactive for them.

States 9 to 15 are invalid states. If counter enters any of these states then it will reset all flip-flops


STEP 3: K-Map

$Q_A Q_B$
 $Q_D Q_C$


	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	0	0	0	0
10	1	0	0	0

$$Y = \bar{Q}_0 + \bar{Q}_n \cdot \bar{Q}_B \cdot \bar{Q}_C$$

STEP 4 : LOGIC DIAGRAM

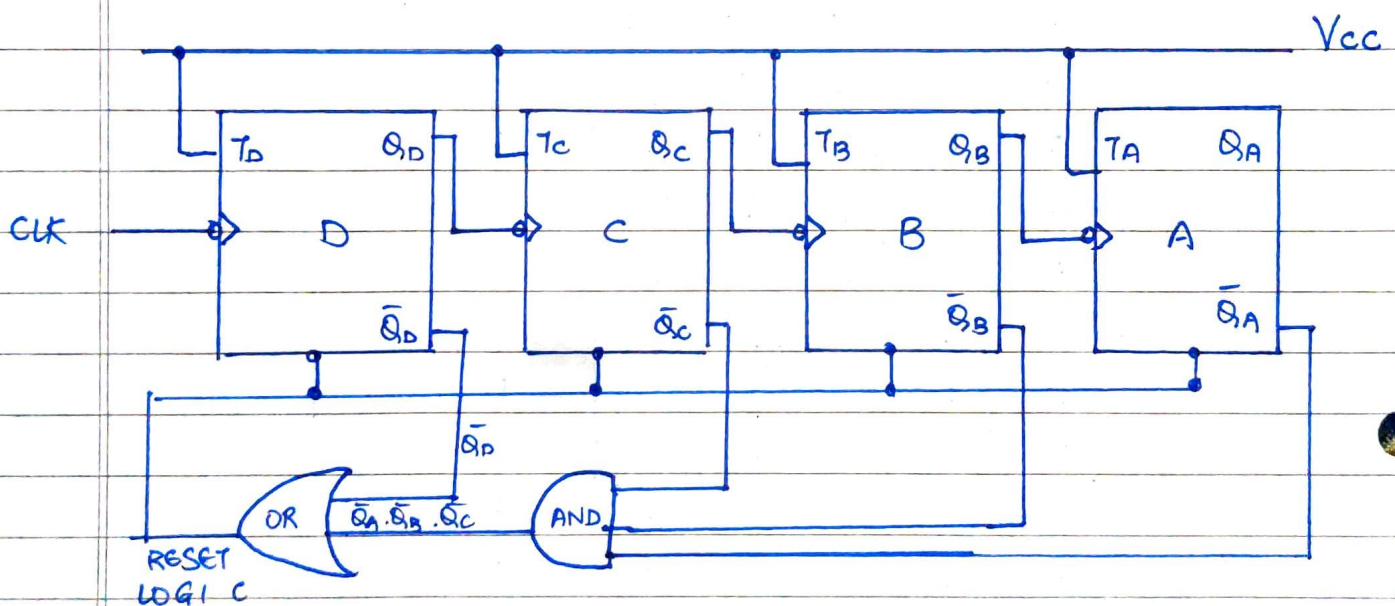

Timing Diagram.

 

Q3

ANS $F(A,B,C,D) = \sum_m (0,1,3,6,9,11,12,13,15)$

The design table is as follows

	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
\bar{A}	(0)	(1)	2	(3)	4	5	(6)	7
A	8	(9)	10	(11)	(12)	(13)	14	(15)

Input to

Multiplexer \bar{A} 1 0 1 A A \bar{A} \bar{A}

The corresponding logic diagram is.

