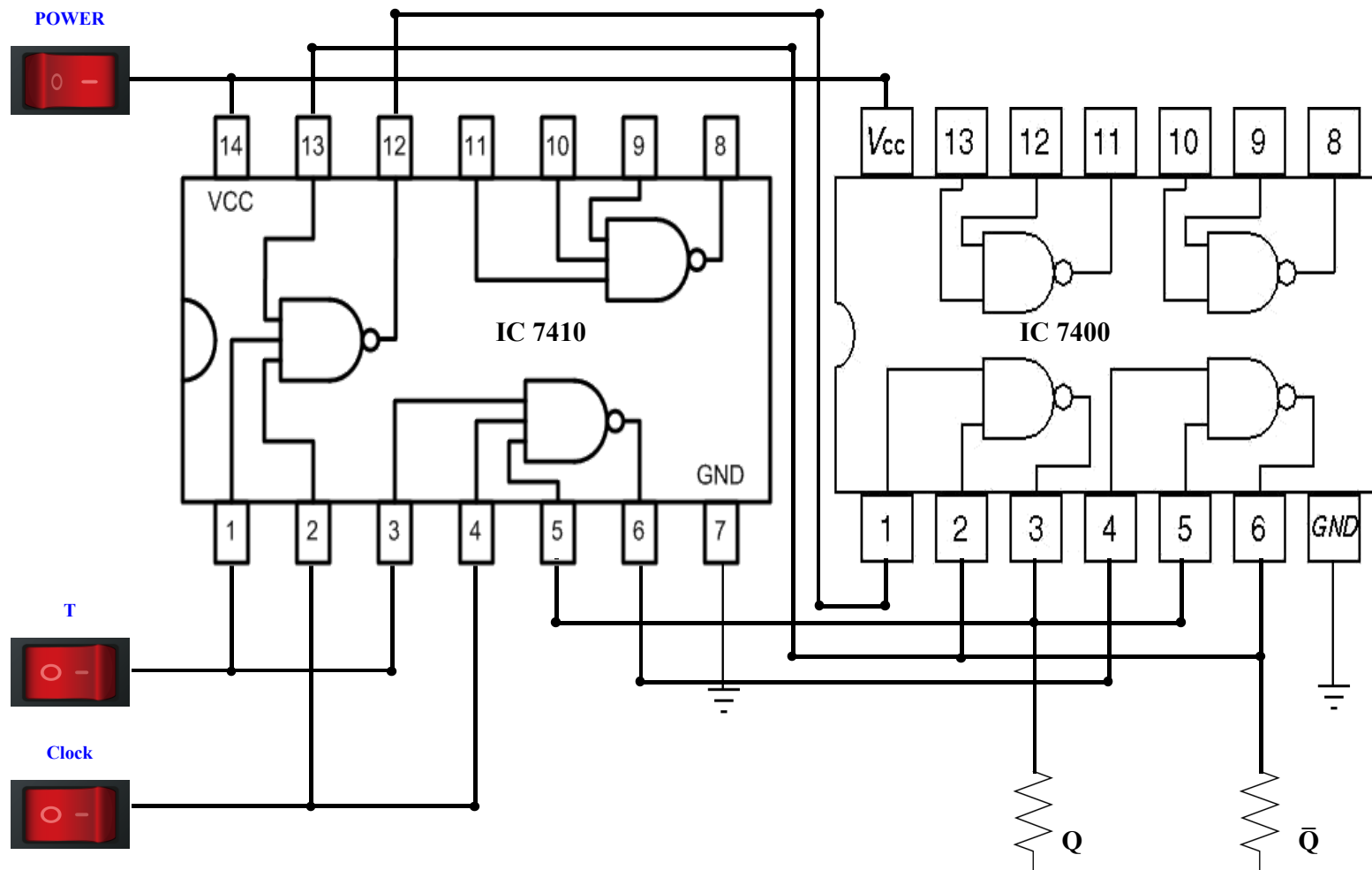


INSTRUCTIONS

Experiment to perform T Flip Flop on kit



TRUTH TABLE

Add

Print

Serial No.	Clock	T	Q_{n-1}	\bar{Q}_{n-1}	Q	\bar{Q}	Remarks
1	0	0	X	X	0	1	No Change
2	0	1	0	1	0	1	No Change
3	1	0	0	1	0	1	No change
4	1	1	0	1	1	0	Toggle

TIMING DIAGRAM

